

## 4. Instruction Execution (Multi-Cycle Implementation)

# Contents

4.1 Limitation of Single-Cycle Implementation

4.2 Multi-Cycle Implementation

# 4.1 Limitation of Single-Cycle Implementation


- Different types of instructions typically need different number of computation steps.

Stage	<b>rrmov rA,rB = 2 0 rA rB</b>	
Fetch	<i>icode, ifun</i>	$icode:ifun \leftarrow M_1[PC]$
	<i>rA, rB</i>	$rA:rB \leftarrow M_1[PC + 1]$
	<i>valC</i>	
	<i>valP</i>	$valP \leftarrow PC + 2$
Decode	<i>valA, srcA</i>	$valA \leftarrow R[rA]$
	<i>valB, srcB</i>	
Execute	<i>valE</i>	$valE \leftarrow valA + 0$
	<i>cond</i>	
Memory	<i>valM</i>	
Write back	<i>dstE</i>	$R[rB] \leftarrow valE$
	<i>dstM</i>	
PC update	<i>PC</i>	$PC \leftarrow valP$

Stage	<b>jXX = 7 X D</b>	
Fetch	<i>icode, ifun</i>	$icode:ifun \leftarrow M_1[PC]$
	<i>rA, rB</i>	
	<i>valC</i>	$valC \leftarrow M_4[PC + 1]$
	<i>valP</i>	$valP \leftarrow PC + 9$
Decode	<i>valA, srcA</i>	
	<i>valB, srcB</i>	
Execute	<i>valE</i>	
	<i>cond</i>	$branch \leftarrow Check(cond, ifun)$
Memory	<i>valM</i>	
Write back	<i>dstE</i>	
	<i>dstM</i>	
PC update	<i>PC</i>	$PC \leftarrow valC \text{ if } (branch = 1) \text{ else } valP$

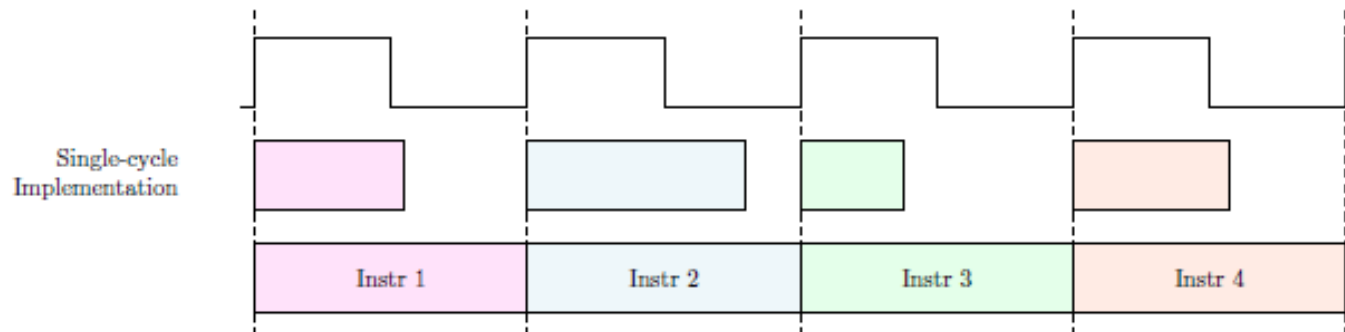
## 4.1 Limitation of Single-Cycle Implementation

- The single – cycle implementation is designed to use only one cycle for every type of instructions.
- The clock period needs to cover all the computation steps, although many instructions need only subset of the steps.
- The performance of the processor can be improved if we can shorten the execution period for some types of instructions.


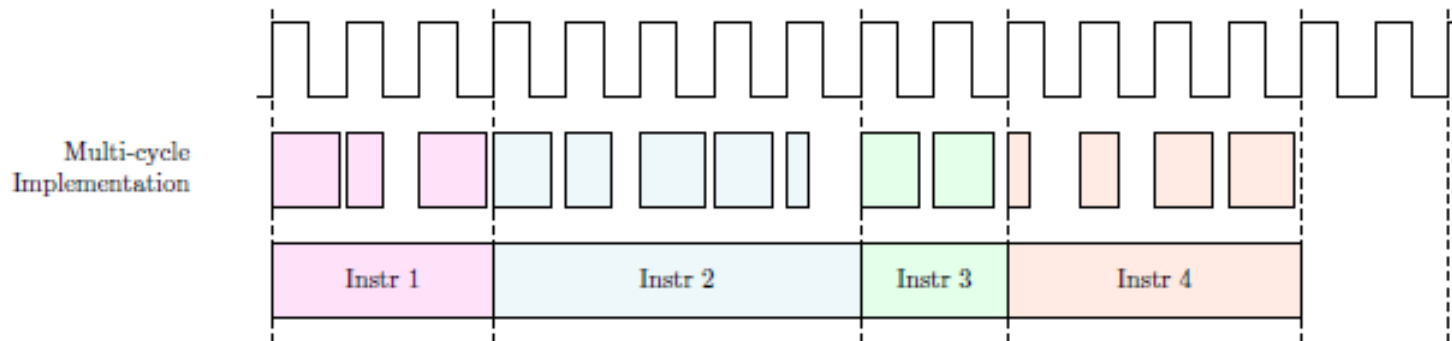
## 4.2 Multi-Cycle Implementation

- The multi – cycle implementation is designed to perform only subset of the computation steps in one cycle.
- Therefore, the clock period can be made shorter than the clock period of the single – cycle implementation.
- However, a single instruction needs multiple cycles to complete all the required steps.



## 4.2 Multi-Cycle Implementation

- In the multi – cycle implementation, all types of instructions do not need to use the same number of cycles for the execution.
- Simple instructions can be executed in a fewer number of cycles than sophisticated instructions.
- Thus, this improves the performance of the processor.

## 4.2 Multi-Cycle Implementation

### **Single – cycle implementaion**

- One clock cycle is for executing one instruction.
- Every instruction type requires the same execution time.

### **Multi – cycle implementation**

- One clock cycle is for executing one stage.
- Different instruction types require different number of cycles, i.e. different execution time.


## 4.2.1 Datapath

- We need to introduce a number of **temporary storages** in the datapath.
- They are necessary to store the values through the multiple cycles that an instruction is executed.
- We set these new control signals to “1” when we want to update the temporary storages in the next cycle.
- If we set them to “0”, the values of the temporary storages remain unchanged.




## 4.2.1 Datapath

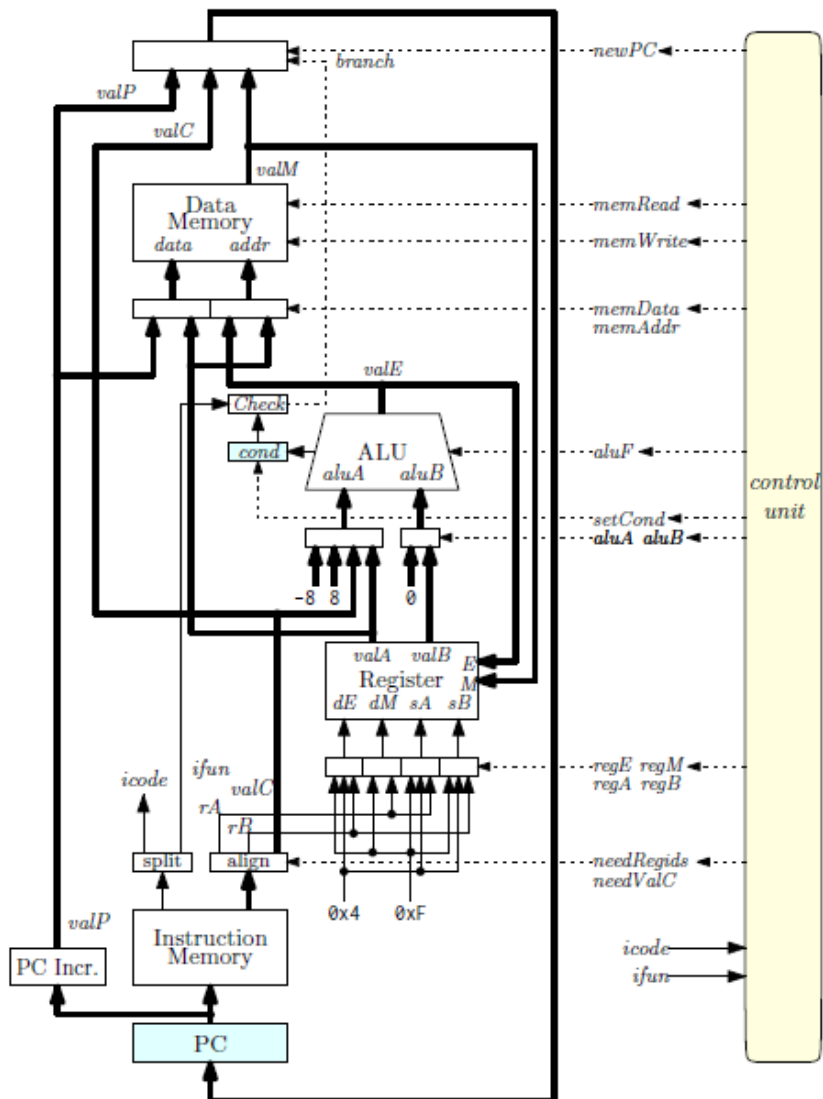1. Instruction Register – it is used to stored the fetched instruction.  
The irWrite control signal – it can be set to 1 when the register needs updating.
2. valP and valPWrite – they are a storage and a control signal for the address of the next instruction.
3. valA and valB – they are storages from the values obtained from the register file.  
valAWrite and valBWrite – we use them to control the updating.
4. valE and valM – They are storages as well.  
valEWrite and valMWrite – we use them to control the updating.
5. pcWrite control signal – it is added to update the PC only the cycle performing PC Update.



## Single – Cycle Implementation

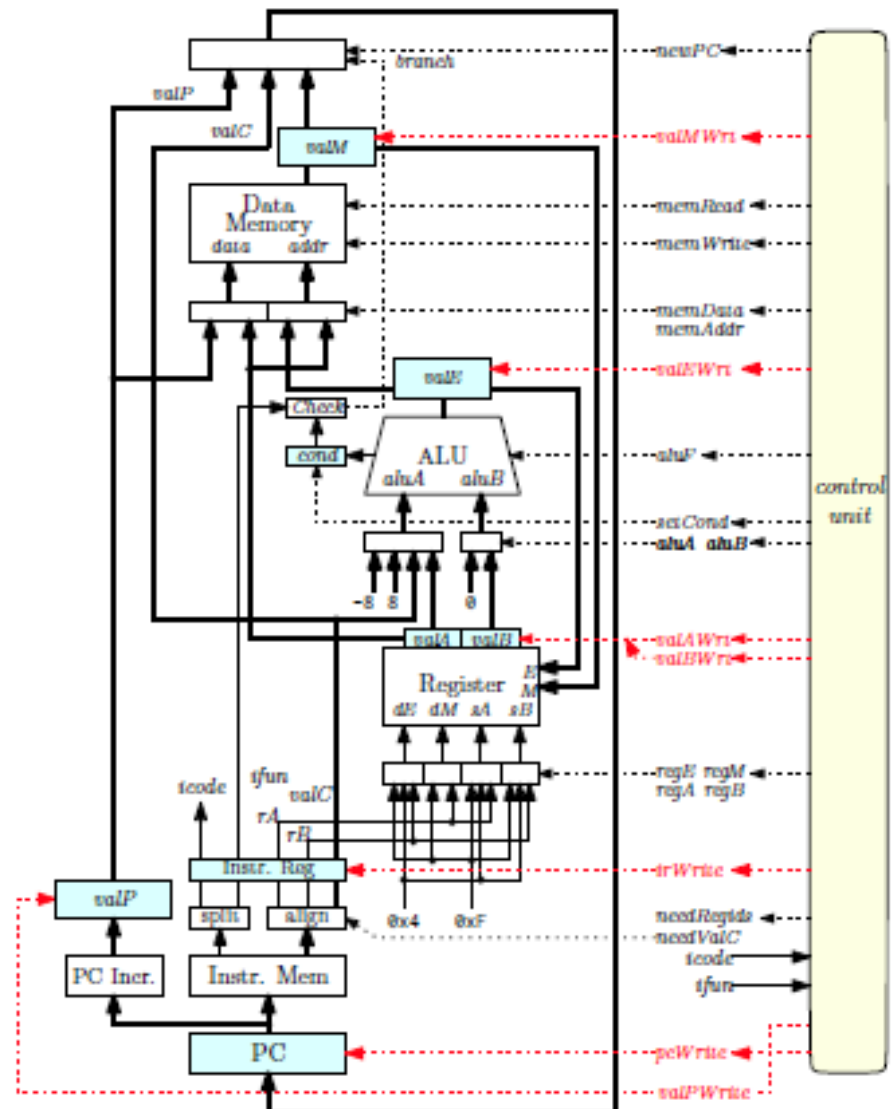

## Multi - Cycle Implementation

# Example 4.1

- Show how a nop instruction is executed.

## Example 4.2


- Show how a `irmov V,rB` instruction is executed.

# Exercise 4.1

- Write the control signal when `mrmov D(rB),rA` is executed.

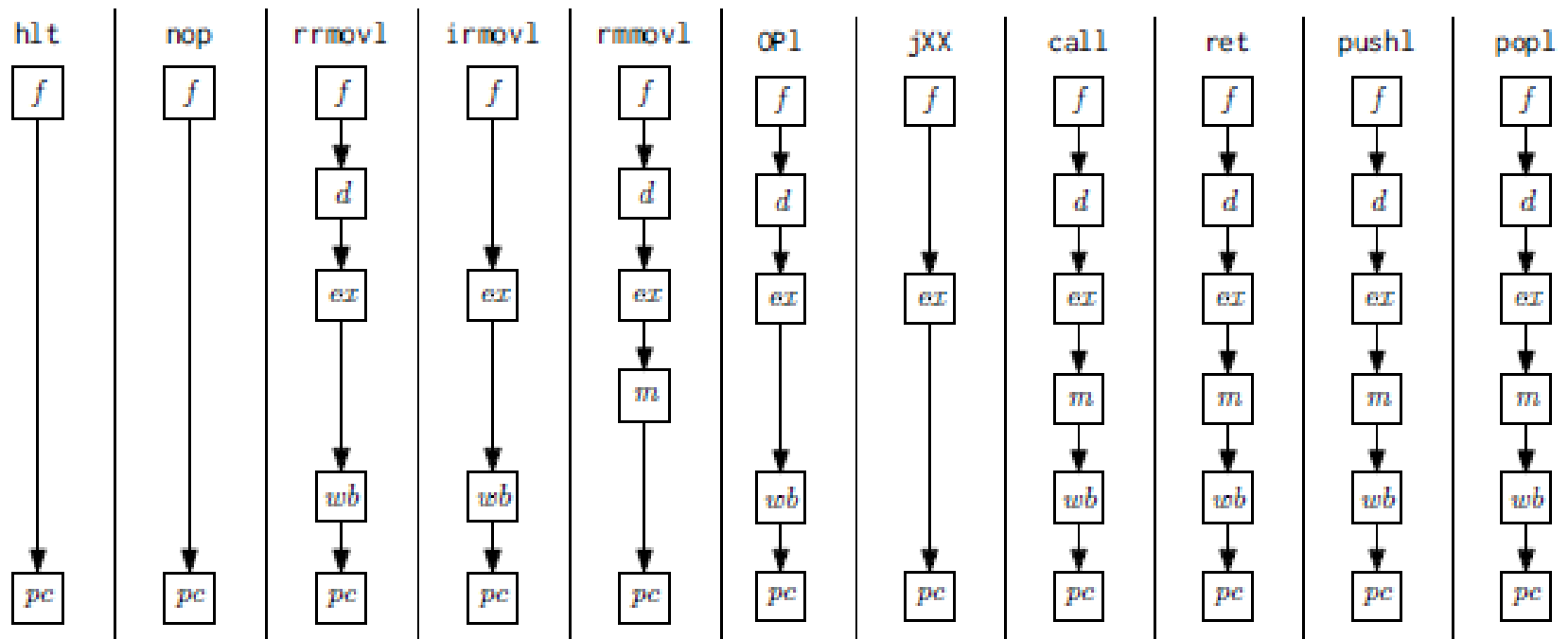
## 4.2.2 Control Unit

- To design a control unit for the multi – cycle implementation, we first need to check how each type of instruction is executed.
- The following figure summarizes the execution stages used in each type of instructions.



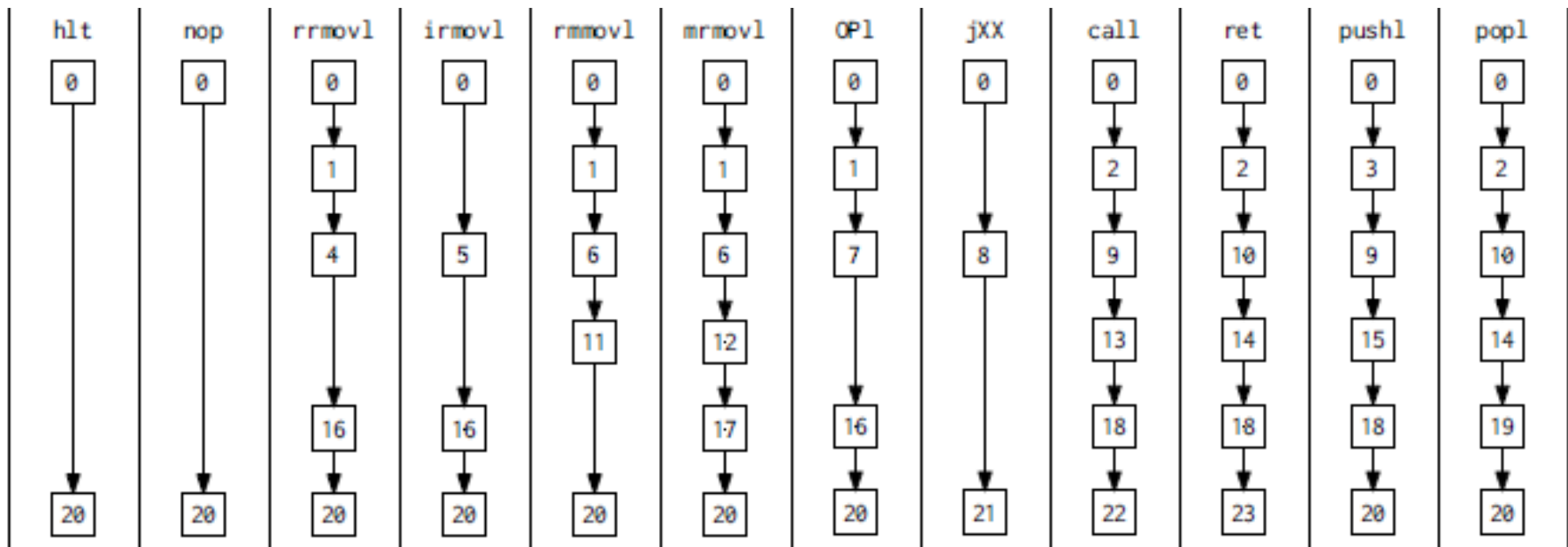
## 4.2.2 Control Unit

- Then, we assign a state number to each computation steps.
- We use the same number for the steps performing the same or similar task.


 
## 4.2.2 Control Unit

- The control unit can be designed as a state machine that emits the control signals based on the current state and the instruction code (icode).
- This can be later transformed to a synchronous digital circuit for the control unit.





## 4.2.3 Determining Clock Period

### Single – cycle implementation

- The clock period (P) needs to be long enough to complete all the stages in the entire datapath.

$$P = P_f + P_d + P_e + P_m + P_{wb} + P_{pc}$$

- CPI (Clock cycle per instruction) = 1

### Multi – cycle implementation

- The clock period needs to be long enough to complete the longest stage in the datapath.

$$P = \max \{P_f, P_d, P_e, P_m, P_{wb}, P_{pc}\}$$

## 4.2.3 Determining Clock Period

- Exercise 4.3 From the following required time period for each computation stage, what are the clock period for the single – cycle and multi – cycle implementation of Y86?

Stage	Required Time Period
Fetch	0.3 ns
Decode	0.2 ns
Execute	0.3 ns
Memory	0.4 ns
Write back	0.2 ns
PC Update	0.1 ns

## 4.2.3 Determining Clock Period

- Exercise 4.4 What is the execution time and CPI of the following program when the clock period is set to 0.5 ns?

```
push %rbx
push %rsi
irmov $0,%rbx
irmov $5,%rsi
add %rbx,%rsi
pop %rsi
pop %rbx
ret
```

## 4.3 Microprogramming

- A simple technique used to implement the control units is called “hardwired control implementation”.
- This technique has a limitation that changing a part in the datapath causes the circuit to be redesigned.
- Another technique is called “microprogramming”. This is a technique to implement the control units by using ROM to store the collection of control signals corresponding to the state, as well as the next state.
- Therefore, the control unit can be changed without redesigning the entire circuit.

# References

- C.Nattee, Lecture Note of CSS224 Computer Architectures, 2017.